

I PUC MID-TERM EXAMINATION, OCTOBER-2023 (SET-2)

Time : 3 Hrs. 15 Mins.

SUBJECT : ELECTRONICS (40)

Max. Marks : 70

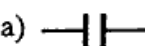
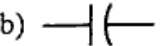

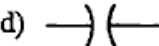
Instructions:

1. The question paper has four parts : A, B, C and D.
2. Part-A is compulsory.
3. Part-D consists of Section-I Essay type questions and Section-II problems.
4. Circuit diagrams and truth tables must be drawn wherever necessary.
5. Solve the problems with relevant formulae.

PART-A

I Select the correct answer from the choices given :

15x1=15

- 1) Vacuum tube diode was invented by
a) Lee De Forest b) Shockley c) J. A. Fleming d) Jack Kilby
- 2) Most commonly used semiconductor material in device fabrication is,
a) Silicon b) Germanium c) Aluminium d) Boron
- 3) For the invention of transistor in 1956 three scientists are awarded by
a) Padmashri b) Padmavibhushana c) Padmabhushana d) Nobel
- 4) The SI unit of charge is
a) Volt b) Ampere c) Ohm d) Coulomb
- 5) Number of electrons in coulomb of charge is
a) 6.25×10^5 b) 6.25×10^2 c) 6.25×10^{18} d) 6.25×10^{19}
- 6) Internal resistance of an ideal voltage source is
a) 0Ω b) $1 \text{ M}\Omega$ c) $10 \text{ k}\Omega$ d) ∞
- 7) One kilowatt-hour is
a) $3.6 \times 10^{16} \text{ J}$ b) $3.6 \times 10^6 \text{ J}$ c) $3.6 \times 10^{18} \text{ J}$ d) $36 \times 10^6 \text{ J}$
- 8) The value of the resistor if colour bands are Brown, Black, Red and Gold
a) $1 \text{ k}\Omega \pm 10\%$ b) $1 \text{ k}\Omega \pm 20\%$ c) $10 \text{ k}\Omega \pm 5\%$ d) $1 \text{ k}\Omega \pm 5\%$
- 9) Symbol of an electrolytic capacitor is
a)  b)  c)  d) 
- 10) Expression for energy stored in a capacitor is
a) 2 CV^2 b) $\frac{1}{2} \text{ C}^2 \text{ V}$ c) $2 \text{ C}^2 \text{ V}$ d) $\frac{1}{2} \text{ C}^2 \text{ V}$
- 11) Value of an SMD resistor marked as 6R5 is
a) 65Ω b) $65 \text{ k}\Omega$ c) 6.5Ω d) $65 \times 10^{12} \Omega$
- 12) Pentavalent dopants are also known as
a) acceptor impurity b) donor impurity c) Insulators d) conductors
- 13) Knee voltage for the germanium diode will be
a) 3.3V b) 0.7V c) 0.3V d) 7.7V
- 14) PIV of a Half wave rectifier is
a) $2V_m$ b) $\frac{2}{\pi} V_m$ c) $\frac{V_m}{\pi}$ d) V_m
- 15) Number of diodes used in Bridge rectifier is
a) 4 b) 3 c) 2 d) 1

II Fill in the blanks by choosing appropriate answers from those given in the bracket: 5x1=5
[a] Lithium-ion battery b) Variable c) Electron Volt d) depletion region e) Hertz]

16) _____ is the unit of frequency.

17) An example for secondary DC source is _____.

(P.T.O)


- 18) Potentiometer is a _____ resistor
- 19) Energy gap is measured in _____.
- 20) The region near the junction where there is no free electrons and holes is _____.

PART-B

III Answer any FIVE questions:

5x2=10

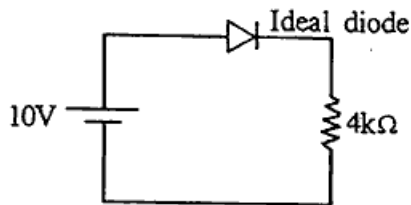- 21) Calculate the number of electrons flowing in a conductor in one second if 4 Amps or current flows through it.
- 22) Find the power consumed by a phone when operated with a 5 Volt and 15 mA of current.
- 23) What are primary DC sources ? Give one example.
- 24) State Super position theorem.
- 25) Define active and passive components.
- 26) Calculate the total capacitance if three capacitors $20\ \mu\text{F}$, $40\ \mu\text{F}$ and $60\ \mu\text{F}$ are connected in series.
- 27) Draw the crystalline structure of n-type semiconductor. <https://www.karnatakaboard.com>
- 28) What are the majority and minorities charge carriers of p-type semiconductors.
- 29) Calculate load voltage and load current for the circuit shown below.




PART-C

IV Answer any FIVE questions:

5x3=15

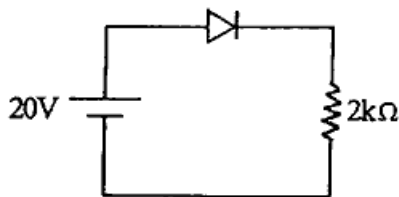- 30) Give a brief note on role of electronics in medical science.
- 31) Mention three applications of cellphone.
- 32) List the properties of charges.
- 33) State and explain KVL.
- 34) Explain current divider rule.
- 35) State Ohm's law and write it's limitations.
- 36) Explain the construction of metal film resistor.
- 37) Draw and explain the V-I characteristics of a p-n junction diode.
- 38) A silicon diode is used in the circuit. Determine V_D , V_R , I_D .



**PART-D
(SECTION-I)**

V Answer any THREE questions:

3x5=15


- 39) State and explain Maximum Power Transfer theorem with an example.
- 40) Define the following terms
 - a) Node
 - b) Loop
 - c) Mesh
 - d) Linear Network
 - e) Bi-lateral Network
- 41) Write a note on colour code chart of a resistor.
- 42) Explain the principle of a capacitor.
- 43) With a relevant circuit diagram and input and output waveforms explain the working of centre tapped full wave Rectifier.
- 44) Classify solids based on energy band diagram.

(SECTION-II)


VI Answer any TWO questions:

2x5=10

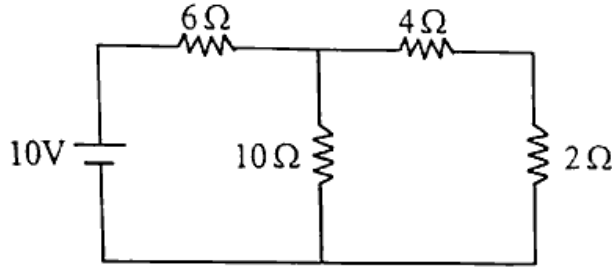45) Determine the branch currents and voltage drops across each resistor.



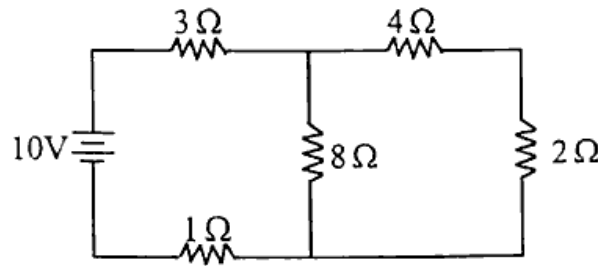46) Find the current through and voltage across 2Ω resistor using Thevenin's theorem.



47) A half-wave rectifier uses a diode with forward resistance $40\ \Omega$. If the input ac voltage is $220\ V_{rms}$ and the load resistance is $10\ k\Omega$, determine

- (i) I_m
- (ii) I_{dc}
- (iii) Peak inverse voltage
- (iv) Load output voltage
- (v) DC output power.

48) A $230\ V$, $50\ Hz$ AC voltage is applied to the primary of $4 : 1$ step down transformer, which is used in bridge rectifier having a load resistance of $100\ \Omega$. Assuming the diodes to be an ideal determine,

- (i) Peak supply voltage
- (ii) I_{dc}
- (iii) V_{dc}
- (iv) P_{dc}
- (v) PIV.

<https://www.karnatakaboard.com>

Whatsapp @ 9300930012

Send your old paper & get 10/-

अपने पुराने पेपर्स भेजे और 10 रुपये पायें,

Paytm or Google Pay से